

# Analog 12.7.4

EE1205 : Signals and Systems  
Indian Institute of Technology Hyderabad

Chirag Garg  
(EE23BTECH11206)

**Question:** A  $60 \mu F$  capacitor is connected to a  $110 V, 60 Hz$  ac supply. Determine the rms value of the current in the circuit. The  $I_{rms}$  value is defined as :-

**Solution:**

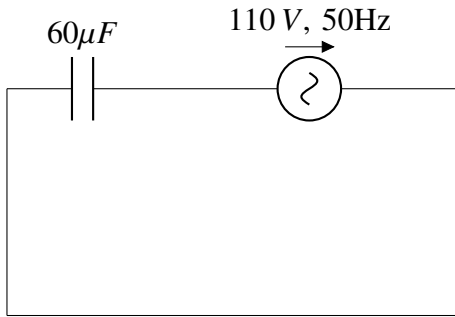


Fig. 1

Symbol	Value	Description
$C$	$60 \mu F$	Capacitance
$V_0$	$110 \sqrt{2} V$	Peak Voltage
$I_0$	$V_0 \times \omega C$	Peak Current
$f$	$60 Hz$	Frequency
$\omega$	$2\pi f$	Angular Frequency
$H(s)$	$\frac{V(s)}{I(s)}$	Transfer Function

Table 1 : Given Parameters

The voltage as a function of time can be given as :

$$V(t) = V_0 \cos(\omega t) \quad (1)$$

So the current as a function of time will be given as :

$$I(t) = V_0 \times \omega C \cos(\omega t + \frac{\pi}{2}) \quad (2)$$

$$= I_0 \sin(\omega t) \quad (3)$$

$$I_{rms}^2 = \frac{1}{T} \int_0^T [I(t)]^2 dt \quad (4)$$

$$= f \int_0^{\frac{1}{f}} I_0^2 \cdot \sin^2(2\pi f t) dt \quad (5)$$

$$= \frac{1}{2} I_0^2 \left( 1 - \frac{1}{f} \left[ \frac{\sin(4\pi f t)}{4\pi f} \right]_0^{\frac{1}{f}} \right) \quad (6)$$

$$= \frac{1}{2} I_0^2 \left( 1 - \frac{1}{f} \cdot \frac{\sin(4\pi) - \sin(0)}{4\pi f} \right) \quad (7)$$

$$= \frac{I_0^2}{2} \quad (8)$$

$$I_{rms} = \frac{I_0}{\sqrt{2}} \quad (9)$$

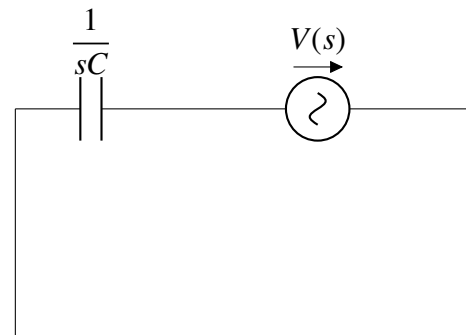


Fig. 2 : Equivalent s domain circuit

We know that,

$$H(s) = \frac{1}{sC} \quad (10)$$

$$= \frac{1}{j\omega C} \quad (11)$$

$$|H(j\omega)| = \left| \frac{1}{j\omega C} \right| \quad (12)$$

$$= \frac{1}{(2\pi) \times (60) \times (60) \times (10^{-6})} \quad (13)$$

$$\approx 44.21 \quad (14)$$

$$I(s) = \frac{V(s)}{H(s)} \quad (15)$$

$$= \frac{110}{44.21} \quad (16)$$

$$\approx 2.49A \quad (17)$$